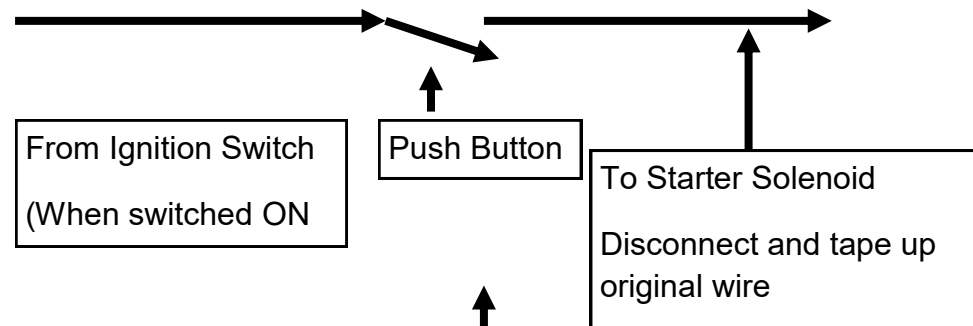


Heater Circuit



Starter Circuit

Parts required

1 Heavy Duty Relay—Ebay or Amazon

2 Push buttons (Momentary!)

Circa 2 metres 10 amps wire

Lucar Connectors/Terminals

I simply disconnected and left the controller in situ.

I used a 100 amp relay—about £7- 8

2 Good quality push Buttons.

This has worked perfectly since fitting — used heaters/glow plugs only once!

YOU determine the time, depending on the temperature.